

- **Question:** imagine we need a cyclic n -bit **counter**, i.e., a component whose output r steps through values

$$0, 1, \dots, 2^n - 1, 0, 1 \dots$$

but is otherwise uncontrolled (or “free running”).


Notes:

- **Question:** imagine we need a cyclic n -bit **counter**, i.e., a component whose output r steps through values

$$0, 1, \dots, 2^n - 1, 0, 1 \dots$$

but is otherwise uncontrolled (or “free running”).

 - **Solution (?):** we already have an n -bit adder that can compute $x + y \dots$




Notes:

- **Question:** imagine we need a cyclic n -bit **counter**, i.e., a component whose output r steps through values

$$0, 1, \dots, 2^n - 1, 0, 1 \dots$$

but is otherwise uncontrolled (or “free running”).

 - **Solution (?)**: we already have an n -bit adder that can compute $x + y \dots$



... so we'll just compute $r \leftarrow r + 1$ over and over again; this *sounds* like a good idea, but **won't work** due to (at least) two flaws:

1. we can't initialise the value, and
2. we don't let the output of each full-adder settle before it's used again as an input.

Notes:

- **Actual problem:** combinatorial logic has some limitations, namely we can't
 - control *when* a circuit computes some output (it does so continuously), nor
 - remember the output when produced.
- **Actual solution:** **sequential** logic, which demands
 1. some way to synchronise components in the circuit,
 2. one or more components that remember what state they are in, and
 3. a mechanism to perform computation as a sequence of steps rather than continuously.

Notes:


- Components that remember state can be classified as being either
 1. an **astable**, where the component is not stable in either state and flips uncontrolled between states,
 2. a **monostable**, where the component is stable in one states and flips uncontrolled but periodically between states, or
 3. a **bistable**, where the component is stable in two states and flips between states under control of an input,

Notes:

Clocks (1)

- A **clock** is a signal that oscillates (or alternates) between 1 and 0; we feed it into circuits to synchronise components in them:

Definition (1-phase clock)

 


- **Idea:**
 - The clock **triggers** events, e.g., steps in some sequence of computations.
 - The **clock frequency** is how many clock cycles happen per-second; it has to be
 - fast enough to satisfy the design goals, **yet**
 - slow enough to cope with the critical path of a given step
- i.e., the faster the clock “ticks” the faster we step through the computation, but if it’s too fast we can’t finish one step before the next one starts!

Notes:

Clocks (2)

- ▶ A **n -phase clock** is distributed as n separate signals along n separate wires

Definition (2-phase clock)

 

with a 2-phase instance particularly useful:

1. features in a 1-phase clock, e.g., the clock period, levels and edges, translate naturally to both Φ_1 and Φ_2 ,
2. there is a guarantee that positive levels of Φ_1 and Φ_2 don't overlap, and
3. the behaviour is parameterisable by altering δ_i .

Notes:

Clocks (3)

- ▶ A clock signal is typically
 1. an input which needs to be supplied externally, or
 2. produced internally by a **clock generator**then distributed by a **clock network** (e.g., a H-tree).
- ▶ It can be attractive to multiply or divide the clock (i.e., make it faster or slower):

Algorithm (CLOCK-DIVIDE)

To divide (i.e., slow down) a reference clock clk :


1. initialise a counter c to zero,
2. on each positive edge of clk , increment the counter c , then
3. the $(i - 1)$ -th bit of the counter c acts like the clock divided by 2^i .

So if we let $i = 1$, we get a clock which is

$$\frac{1}{2^i} = \frac{1}{2^1} = \frac{1}{2}$$

the speed (i.e., twice as slow) by looking at the 0-th bit of c .

Example

 

Notes:

- The clock generator is typically a piezoelectric crystal or similar.
- The clock network is a bit like the need to distribute power (via power rails); it's power hungry!

Latches and Flip-Flops (1)

- ▶ We need a component which remembers what state it is in; that is, it
 - ▶ retains some **current state** Q (which can also be read as an output), **and**
 - ▶ can be updated to some **next state** Q' (which is provided as an input)
- essentially meaning it stores a 1-bit value of our choice.

Definition (latch versus flip-flop)

Given a suitable bistable component controlled using an **enable signal** en that determines when updates happen, we say it can be

1. **level-triggered**, i.e., updated by a given level on en , or
2. **edge-triggered**, i.e., updated by a given edge on en .

The former type is typically termed a **latch**, with the latter termed a **flip-flop**.

Definition (active-high versus active-low)

Whether a positive or negative level (resp. edge) of some signal controls the component depends on whether it is **active high** or **active low**; a signal en is often written $\neg en$ to denote the latter case.

Notes:

- Latches are sometimes described as **transparent**: this term refers to the fact that while enabled, their input and output will match because the state (which matches the output) is being updated with the input. Flip-flops are not the same, because their state is only updated at the exact instant of an edge.

Latches and Flip-Flops (2)

Definition (SR-type latch/flip-flop)

An “SR” latch/flip-flop component has two inputs S (or **set**) and R (or **reset**):

- ▶ when enabled and
 - ▶ $S = 0, R = 0$ the component retains Q ,
 - ▶ $S = 1, R = 0$ the component updates to $Q = 1$,
 - ▶ $S = 0, R = 1$ the component updates to $Q = 0$,
 - ▶ $S = 1, R = 1$ the component is meta-stable,
- but
- ▶ when not enabled, the component is in storage mode and retains Q .

The behaviour of the component is described by the truth table

SR-LATCH/SR-FLIPFLOP					
S	R	Current		Next	
		Q	$\neg Q$	Q'	$\neg Q'$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	?	?	0	1
1	0	?	?	1	0
1	1	?	?	?	?

Definition (D-type latch/flip-flop)

A “D” latch/flip-flop component has one input D :

- ▶ when enabled and
 - ▶ $D = 1$ the component updates to $Q = 1$,
 - ▶ $D = 0$ the component updates to $Q = 0$,
- but
- ▶ when not enabled, the component is in storage mode and retains Q .

The behaviour of the component is described by the truth table

D-LATCH/D-FLIPFLOP				
D	Current		Next	
	Q	$\neg Q$	Q'	$\neg Q'$
0	?	?	0	1
1	?	?	1	0

Notes:

Definition (JK-type latch/flip-flop)

A “JK” latch/flip-flop component has two inputs J (or **set**) and K (or **reset**):

- when enabled and
 - $J = 0, K = 0$ the component retains Q ,
 - $J = 1, K = 0$ the component updates to $Q = 1$,
 - $J = 0, K = 1$ the component updates to $Q = 0$,
 - $J = 1, K = 1$ the component toggles Q ,
- but
- when not enabled, the component is in storage mode and retains Q .

The behaviour of the component is described by the truth table

JK-LATCH/JK-FLIPFLOP					
J	K	Current		Next	
		Q	$\neg Q$	Q'	$\neg Q'$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	?	?	0	1
1	0	?	?	1	0
1	1	0	1	1	0
1	1	1	0	0	1

Definition (T-type latch/flip-flop)

A “T” latch/flip-flop component has one input T :

- when enabled and
 - $T = 0$ the component retains Q ,
 - $T = 1$ the component toggles Q ,
- but
- when not enabled, the component is in storage mode and retains Q .

The behaviour of the component is described by the truth table


T-LATCH/T-FLIPFLOP				
T	Current		Next	
	Q	$\neg Q$	Q'	$\neg Q'$
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

Notes:


Latches and Flip-Flops (4)

- Problem #1:** how can we design a simple SR latch?
- Solution:** use two *cross-coupled* NOR gates.


Circuit

 


Example ($S = 0, R = 0$, valid)

 


Example ($S = 0, R = 0$, valid)

 


Example ($S = 1, R = 1$, invalid)

 

Example ($S = 1, R = 0$, valid)

 


Example ($S = 0, R = 1$, valid)

 

Notes:

Latches and Flip-Flops (5)

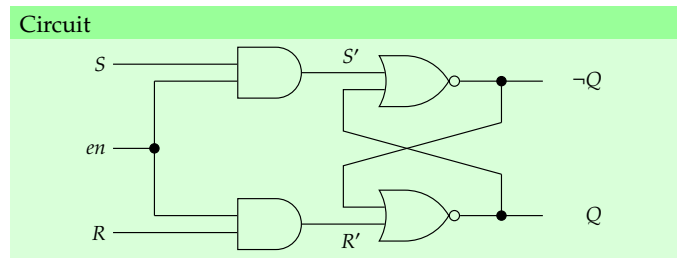- ▶ **Problem #2:** we'd like to control when updates occur.
- ▶ **Solution:** **gate** S and R , controlling whether they act as input to the internal latch.




- ▶ Note that:
 - ▶ The new design is clearly level triggered in the sense S and R are only relevant during a positive level of en , e.g.,
 - ▶ if $en = 0$, $S' = S \wedge en = S \wedge 0 = 0$, whereas
 - ▶ if $en = 1$, $S' = S \wedge en = S \wedge 1 = S$.
 - ▶ If we “gate” a signal more generally, we mean “conditionally turn it off”.

Notes:

Latches and Flip-Flops (6)

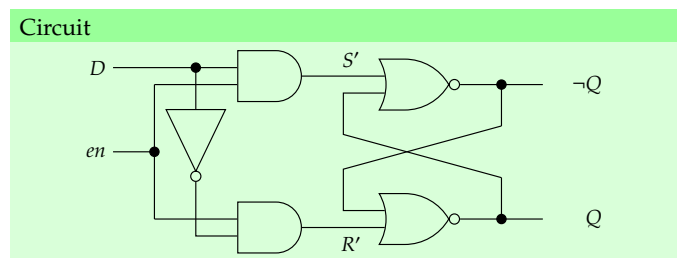- ▶ **Problem #3:** we'd like to avoid the issue of meta-stability.
- ▶ **Solution:** force $R = \neg S$ so either $S = 0$ and $R = 1$, or $S = 1$ and $R = 0$.




- ▶ Note that:
 - ▶ It might *look* like we've *lost* control in that we only have one input D , so cannot retain the current state (i.e., set $S = 0$ and $R = 0$) ...
 - ▶ ... **but** remember:
 1. when $en = 0$ the latch retains Q , and
 2. when $en = 1$ the latch updates Q with D .

Notes:


- ▶ **Problem #4:** the level triggered latch doesn't give very fine grained control over when it is enabled since levels can be quite long.
- ▶ **Solution #1:** "cheat" a bit and construct a **pulse generator** to approximate the idea of edge triggered control.

Circuit

The pulse generator component

 

 is attached to the previous SR latch to give:




Example

Imagine we set the delay of

 1. a NOT gate to 10 ns, and
2. an AND gate to 20 ns

and then flip $en = 0$ to $en = 1$ and back again:




The result is a "pulse" matching the delay of a NOT gate that approximates an edge because it is so short.

Notes:

Latches and Flip-Flops (8)

- ▶ **Problem #4:** the level triggered latch doesn't give very fine grained control over when it is enabled since levels can be quite long.
- ▶ **Solution #2:** adopt a **master-slave** arrangement of two latches

Circuit

 

where the idea is to split a clock cycle into two half-cycles st.

1. while $en = 1$, i.e., during the first half-cycle, the **master** latch is enabled,
2. while $en = 0$, i.e., during the second half-cycle, the **slave** latch is enabled

meaning

- ▶ while $en = 1$, i.e., during a positive level on en , the master latches the input, then
- ▶ exactly as $en = 0$, i.e., a negative edge on en , the slave latches the output from the master


and hence we get an edge triggered component.

Notes:


Latches and Flip-Flops (9)

Definition (D-type latch)

- Written symbolically as

 


- Behaviour is, for example, as follows

 


st. updates are level-triggered by *en*.

Definition (D-type flip-flop)

- Written symbolically as

 

- Behaviour is, for example, as follows

 


st. updates are edge-triggered by *en*.

Notes:

Latches and Flip-Flops (10)

- We typically group such components into **registers**, st. an *n*-bit register can then store an *n*-bit value:

Circuit

 


- Note that:
 - Q_i is the *i*-th bit, for $0 \leq i < n$, of the current value *Q* stored by the register.
 - To **latch** (or store) a some next value Q' , we drive Q'_i onto D_i and wait for *en* to trigger an update.
 - Each component shares a common enable signal, so any such update is therefore synchronised across the whole register.

Notes:

- ▶ We typically group such components into **registers**, st. an n -bit register can then store an n -bit value:

Circuit

 


- ▶ Note that:
 - ▶ Q_i is the i -th bit, for $0 \leq i < n$, of the current value Q stored by the register.
 - ▶ To **latch** (or store) a some next value Q' , we drive Q'_i onto D_i and wait for en to trigger an update.
 - ▶ Each component shares a common enable signal, so any such update is therefore synchronised across the whole register.

Notes:

Conclusions

- ▶ Now we can design a robust solution to the original problem:

Circuit

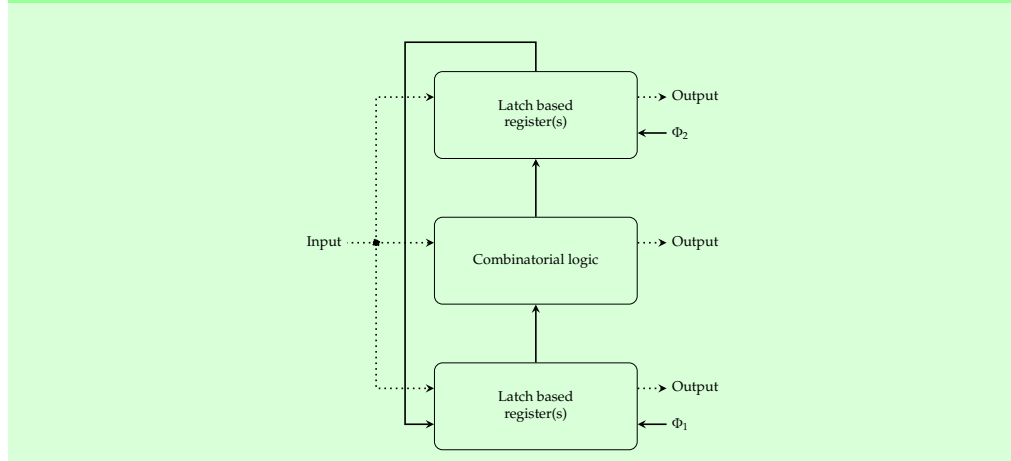

that you can (roughly) view this as a combination of


1. a **data-path**, of computational and/or storage components, and
2. a **control-path**, that tells components in the data-path what to do and when to do it, although here, the control-path is *very* simple ...

Notes:

Conclusions

- Now we can design a robust solution to the original problem:

Circuit

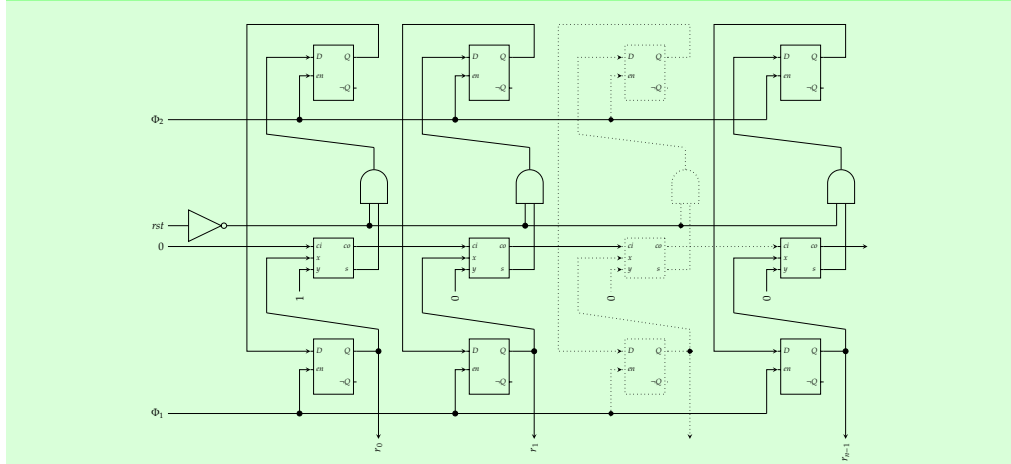

that you can (roughly) view this as a combination of


1. a **data-path**, of computational and/or storage components, and
2. a **control-path**, that tells components in the data-path what to do and when to do it, although here, the control-path is *very* simple ...

Notes:

Conclusions

- Now we can design a robust solution to the original problem:

Circuit

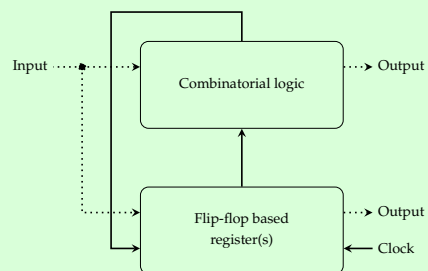

that you can (roughly) view this as a combination of


1. a **data-path**, of computational and/or storage components, and
2. a **control-path**, that tells components in the data-path what to do and when to do it, although here, the control-path is *very* simple ...

Notes:

Conclusions

- Now we can design a robust solution to the original problem:

Circuit

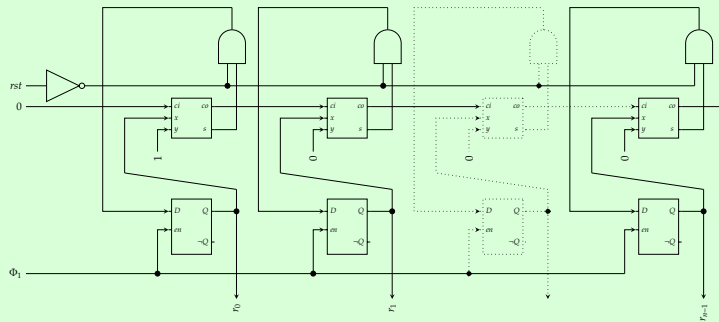

that you can (roughly) view this as a combination of


1. a **data-path**, of computational and/or storage components, and
2. a **control-path**, that tells components in the data-path what to do and when to do it.

although here, the control-path is *very* simple ...

Notes:


Conclusions

Example

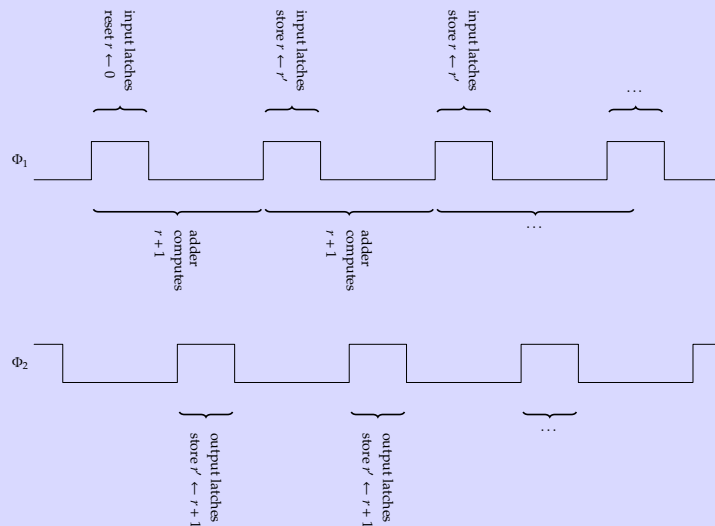

Notes:

Example

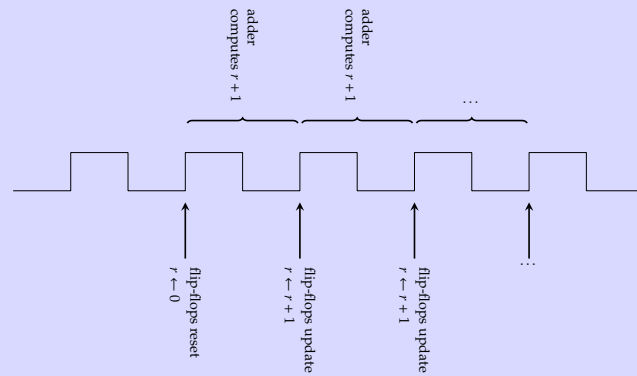

Notes:

Conclusions

► Take away points:

1. The major concept to grasp is the introduction of **time**: not just delay, but step-by-step, controlled rather than continuous, uncontrolled computation.
2. The design of storage, versus computational, components *can* be hard to grasp; probably more important than the detail is the *strategy* ...
3. ... but the control-path in our counter is *very* simple; the next step is to examine how more complex control can be exerted over elements in the data-path.

Notes:

References and Further Reading

- [1] Wikipedia: Clock signal.
http://en.wikipedia.org/wiki/Clock_signal.
- [2] Wikipedia: Flip-flop.
[http://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics)).
- [3] Wikipedia: Latch.
[http://en.wikipedia.org/wiki/Latch_\(electronics\)](http://en.wikipedia.org/wiki/Latch_(electronics)).
- [4] D. Page.
[Chapter 2: Basics of digital logic](#).
In *A Practical Introduction to Computer Architecture*. Springer-Verlag, 1st edition, 2009.
- [5] W. Stallings.
[Chapter 11: Digital logic](#).
In *Computer Organisation and Architecture*. Prentice-Hall, 9th edition, 2013.
- [6] A.S. Tanenbaum.
[Section 3.1: Gates and Boolean algebra](#).
In *Structured Computer Organisation* [8].
- [7] A.S. Tanenbaum.
[Section 3.2: Basic digital logic circuits](#).
In *Structured Computer Organisation* [8].

Notes:

References and Further Reading

- [8] A.S. Tanenbaum.
Structured Computer Organisation.
Prentice-Hall, 6th edition, 2012.

Notes: