

# COMS12200

## Introduction to Computer Architecture


*Simon Hollis (simon@cs.bris.ac.uk)*

COMS12200 Part 6 – Simon Hollis

# STATE MACHINES AND DECODING
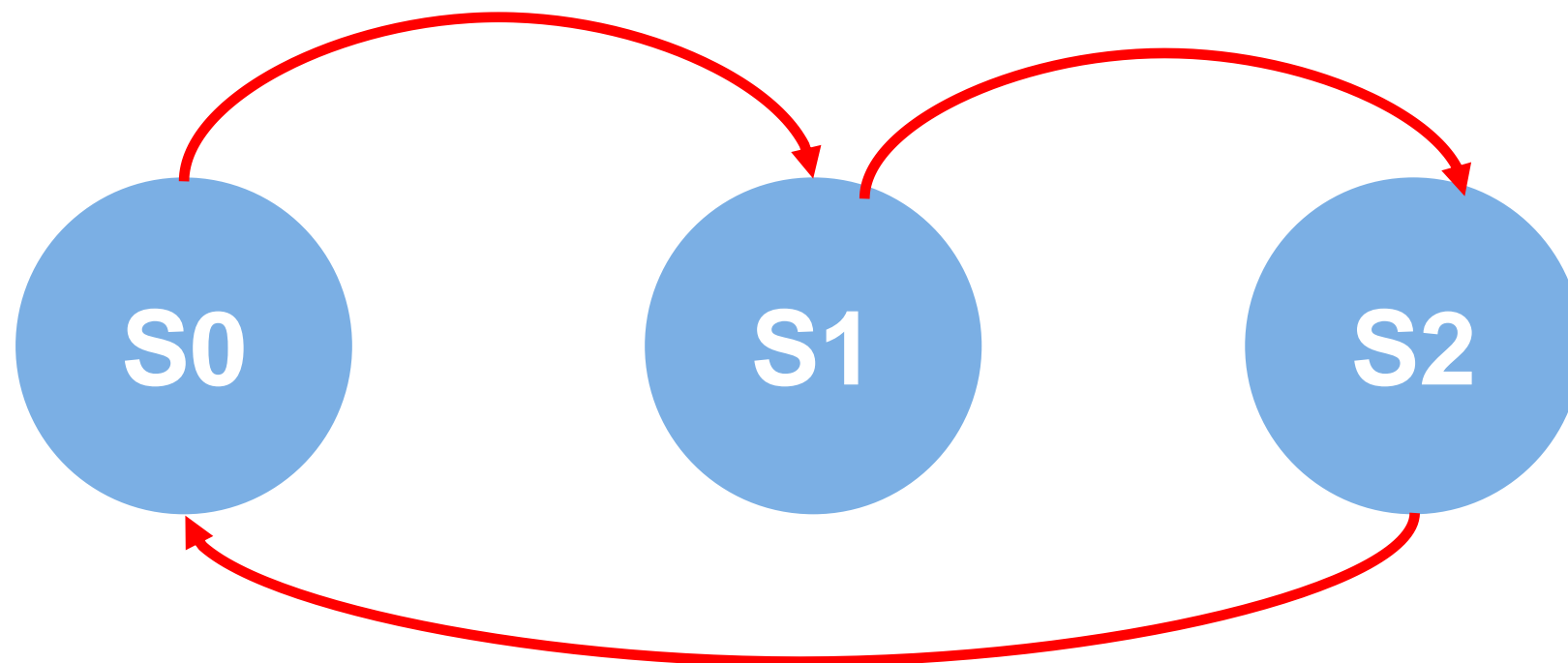
# State machine recap

- A state machine is one with a finite set of defined states.
- Transitions are made between states.
- Transitions can be gated or ungated.



# State machine recap

Each state is uniquely labelled and transitions can also be expressed in a table.


Current state	Next state	Condition
S0	S1	Always
S1	S2	Always
S2	S0	Always

Useful state machines

# TRAFFIC LIGHTS

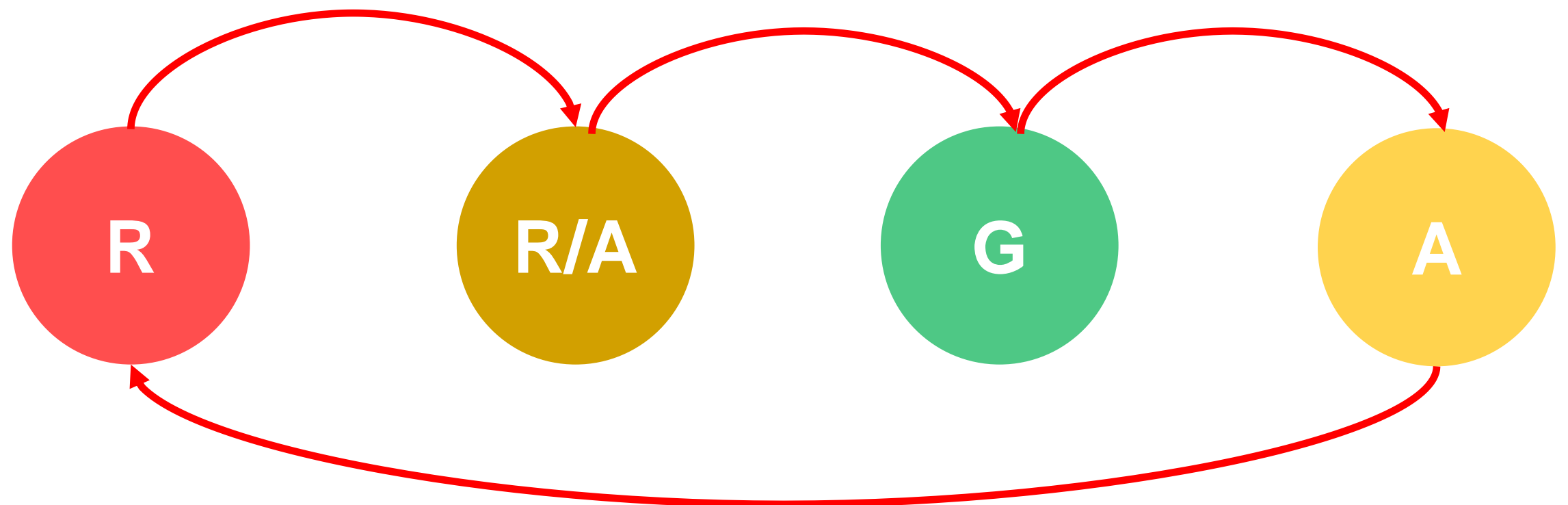
# Traffic lights

A traffic light is a useful state machine with four states



# The simplest four state machine

2 bits = 4 states

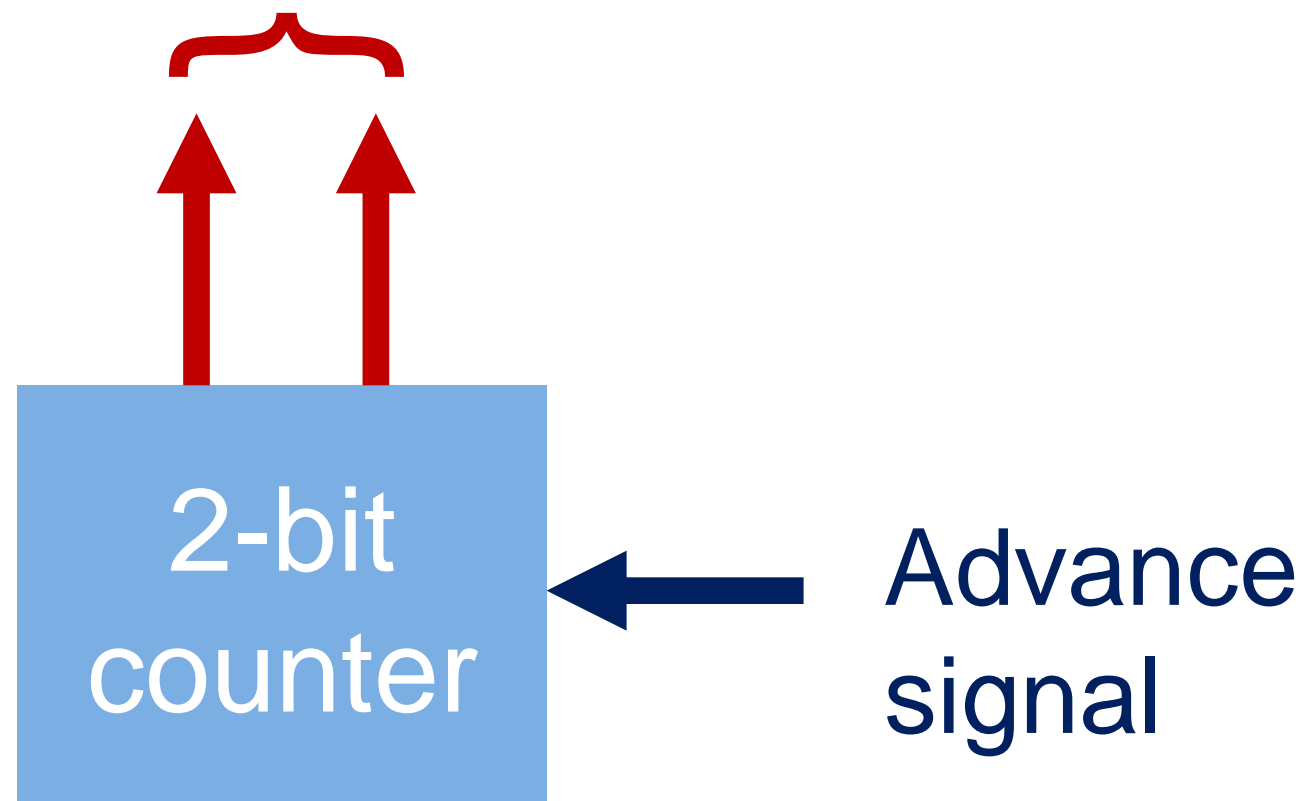


# DECODING STATES


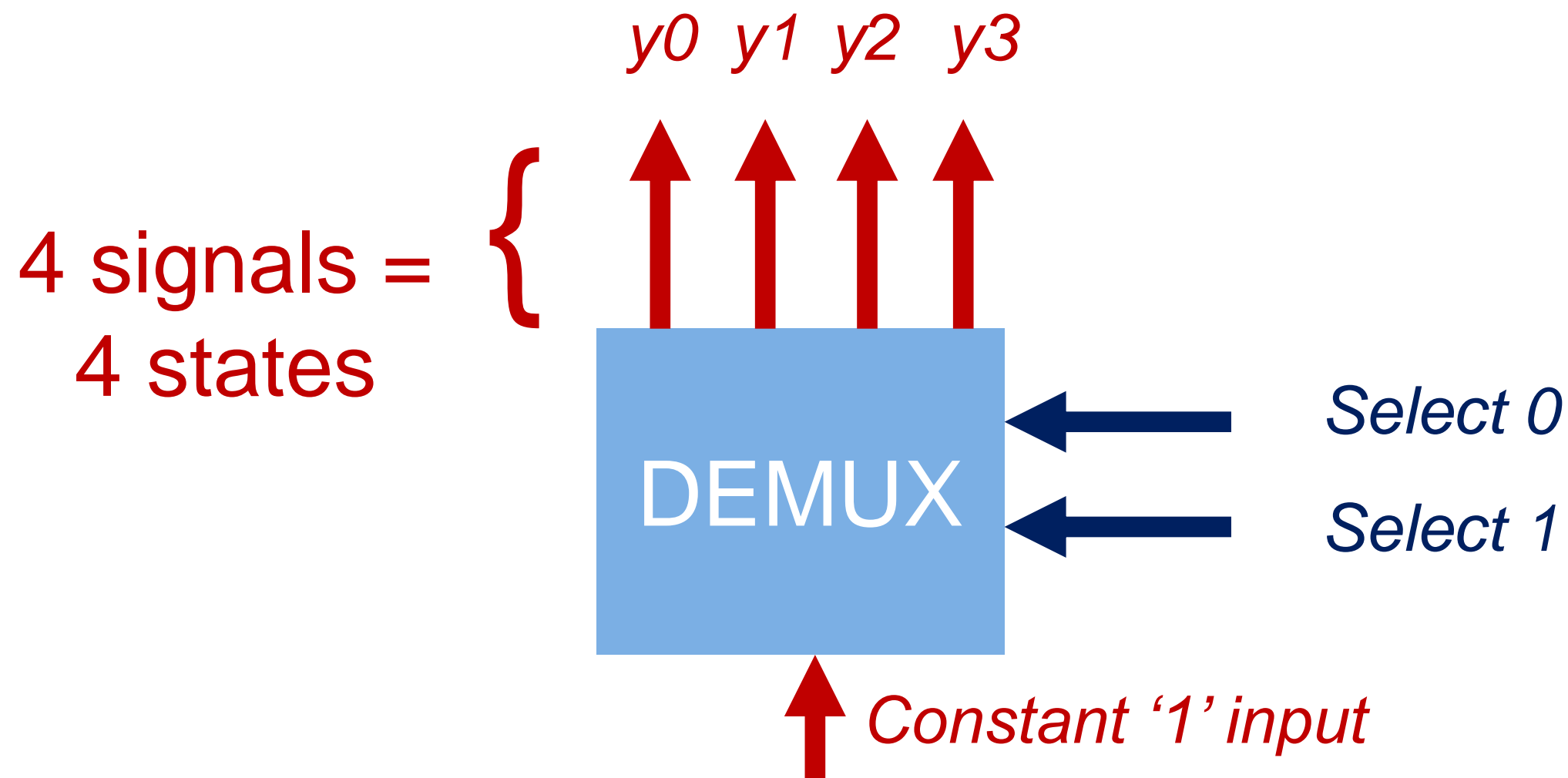
# A four state decoder

- Q: How can we uniquely decode a state from our simple machine?
- A: A DEMUX solves the problem.



# The DEMUX

- How does a DEMUX work?



# From states to lights

- How do we convert the decoder outputs to the R, A, G values for a simple traffic light?



# From states to lights

- Observe that each of the decoder outputs has produced a minterm
- Each minterm is unique and can be manipulated via boolean logic
- Typically, we will combine minterms via logical gates to obtain a compound output (e.g. Red light from R and R/A minterms)

Dynamic behaviour


# VARIABLE CONTROL SIGNALS

# Why vary control?

- In your labs so far, you have made static systems: ones that do the same task again and again.
- To change their behaviour, you have used switches.
- This is great for simple tasks, but we'd really like to be 'hands off' when computing more complex things.
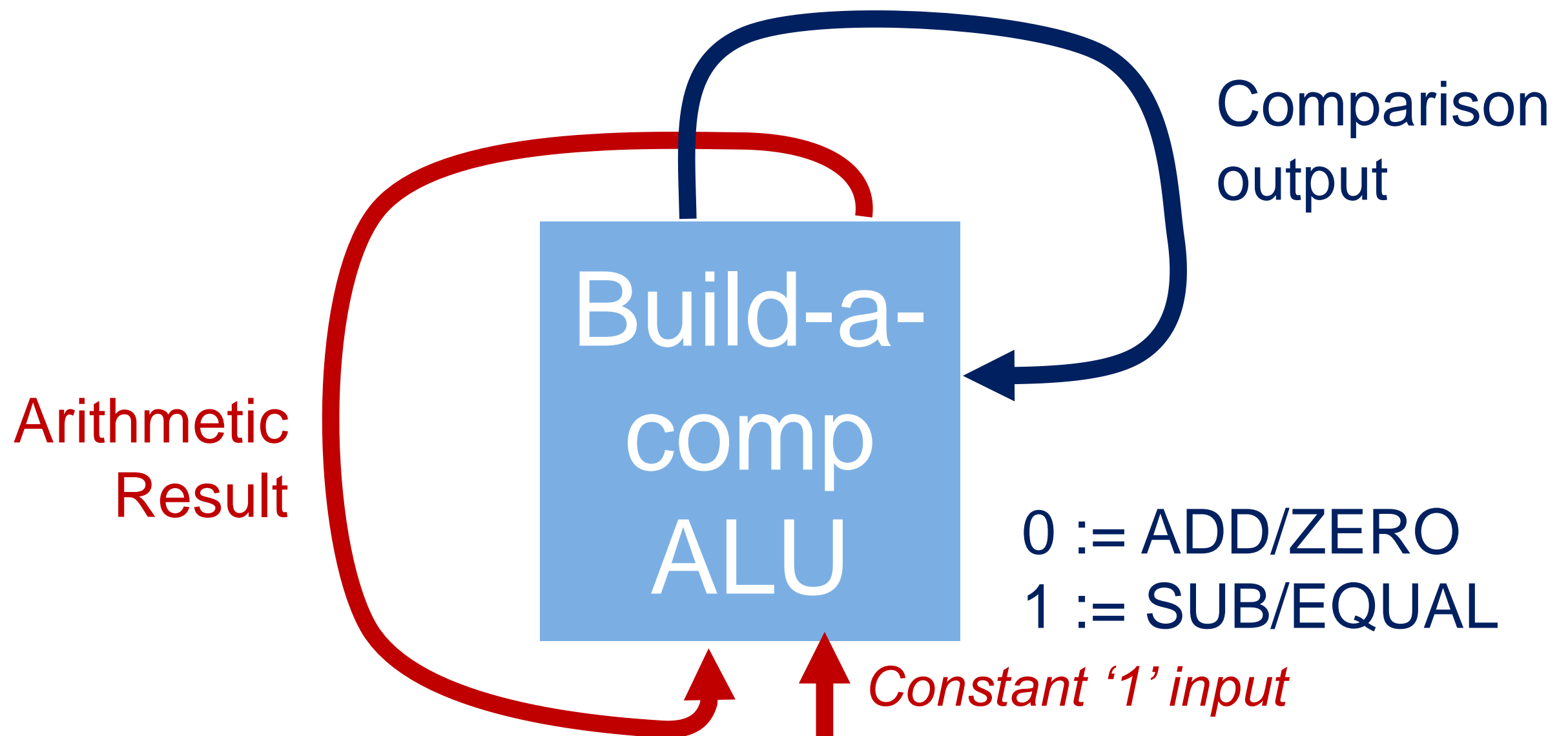
# Supporting variable control

Here's a simple example of how we could vary control to do something useful:



# The notion of feedback

- *Feedback* was the key thing that made the previous example do something interesting.
- Feedback is when a previous output from a system is used to alter its current behaviour:


$$\text{i.e. } S_{n+1} = f(S_n, \text{inputs})$$




# Feedback to change operations

- We can use feedback to alter both the data inputs and/or the function of a unit.
- There are several useful implementation methodologies.
- We'll now look at one simple one (but with a relatively high implementation cost in real systems).

# Changing the data inputs

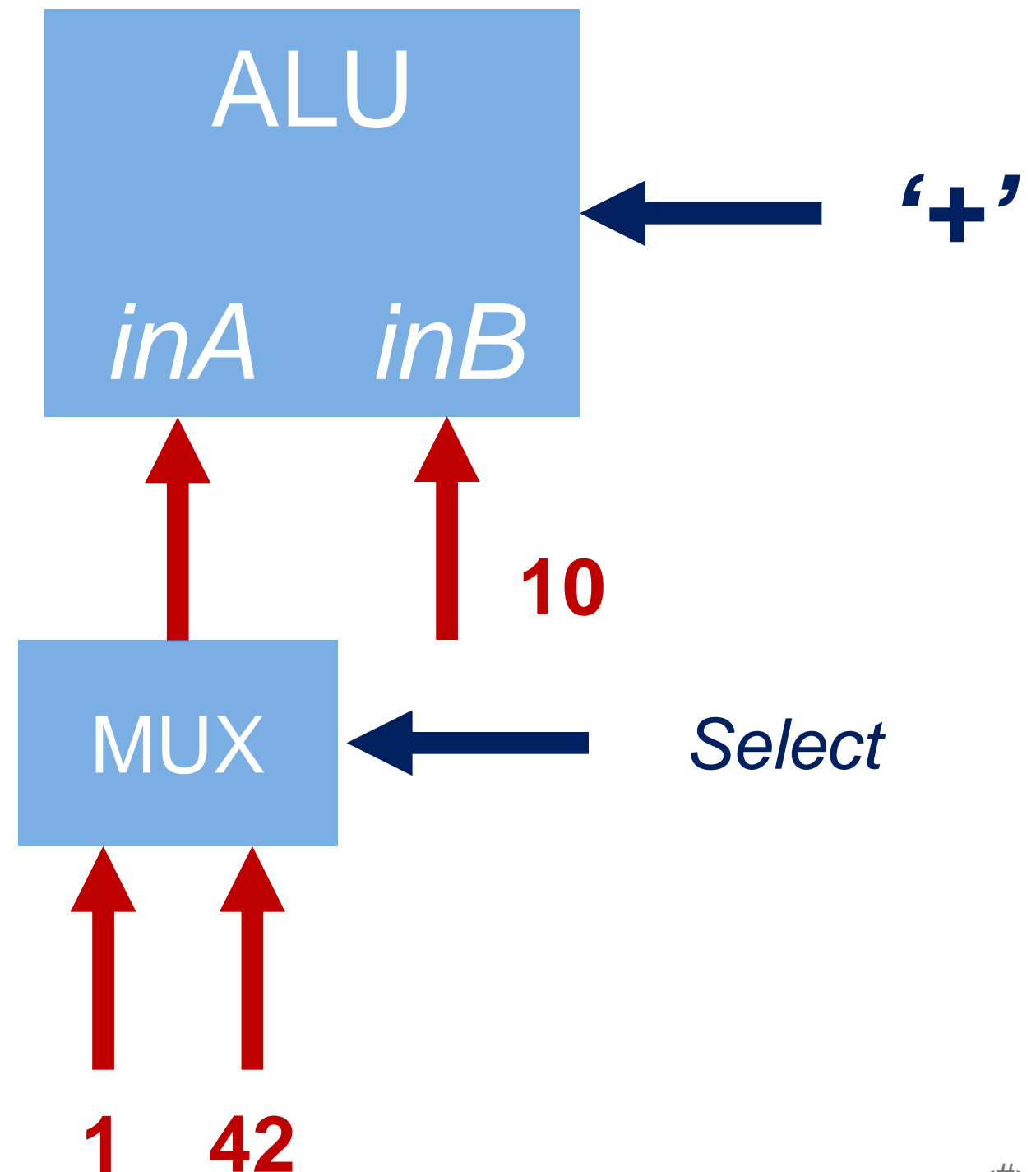

# Changing the control inputs

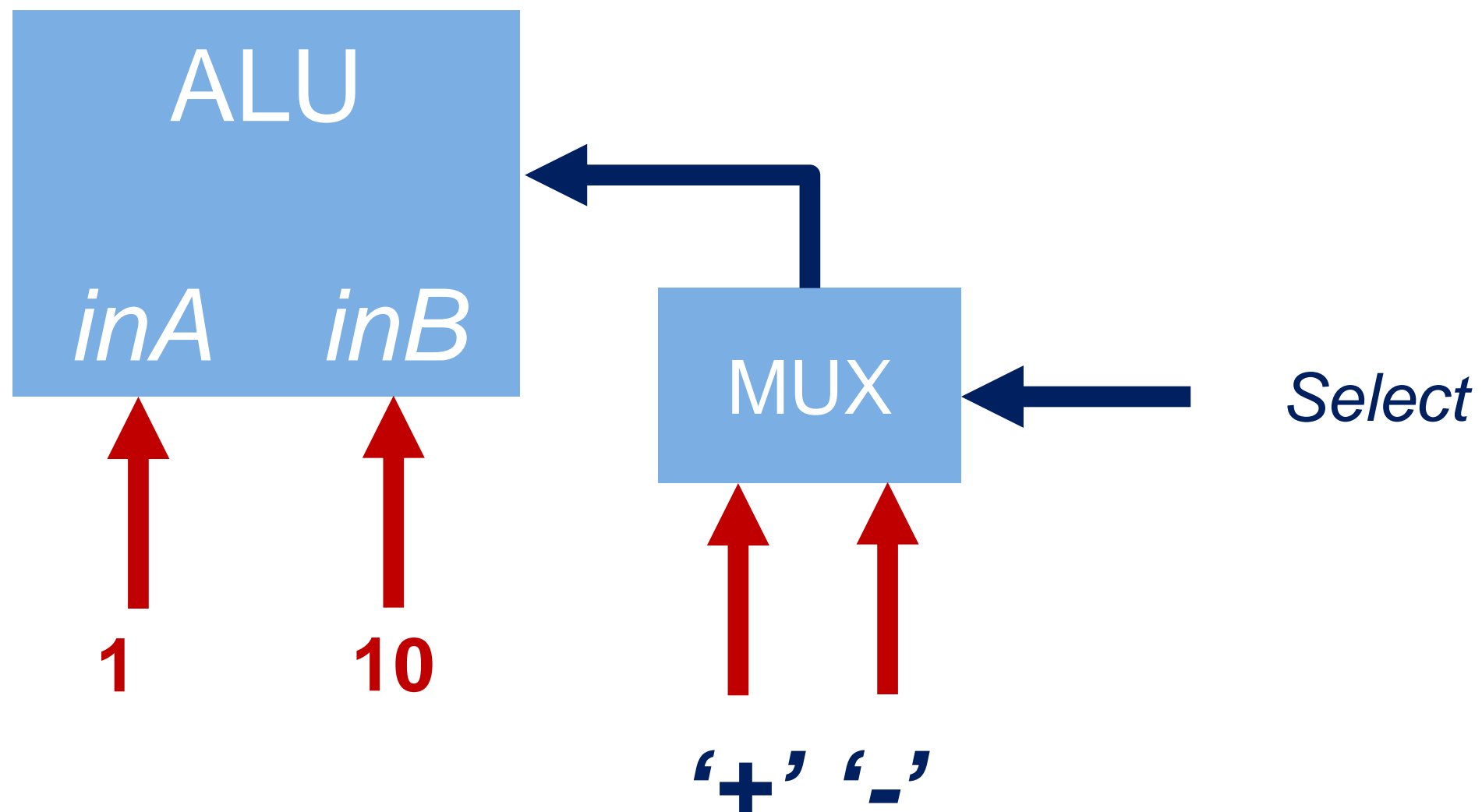

# The MUX

- How does the MUX work?



# Selecting the input

- Where do the *select* signals come from?
- They could come from instructions
  - Instructions will dictate behaviour
- They could come from feedback
  - Data values will dictate behaviour



# Summary

Here are three useful guidelines when creating control flow for state machines:

1. MUXs are useful for selecting inputs
2. DEMUXs are useful for decoding outputs
3. OR gates are useful for combining states and producing feedback signals