

- ▶ The topic of **Finite State Machines (FSMs)** has very formal underpinnings in automata theory ...
- ▶ ... basically they are a model of **computation**:
 - ▶ A FSM is a machine that can be in a finite set of states.
 - ▶ The machine consumes input symbols from an alphabet one at a time; symbols make the machine transition from one state to another according to a transition function.
 - ▶ When the input is exhausted, the machine halts; depending on the state it halts in, the machine is said to accept or reject the input.
 - ▶ The set of inputs accepted by the machine is termed the language accepted; this can be used to classify the machine itself.

Notes:

“Automata Theory in 10 minutes” (1)


Question

Design an FSM that decides whether a binary sequence X has an even or odd number of 0 elements in it.

Algorithm (tabular)

Q	δ	
	Q' $X_i = 0$	$X_i = 1$
S_{even}	S_{odd}	S_{even}
S_{odd}	S_{even}	S_{odd}

Algorithm (diagram)

 

▶ Note that:

1. For the input $X = \langle 1, 0, 1, 1 \rangle$ the transitions are

$$\leadsto S_{even} \xrightarrow{X_0=1} S_{even} \xrightarrow{X_1=0} S_{odd} \xrightarrow{X_2=1} S_{odd} \xrightarrow{X_3=1} S_{odd}$$

so the input is rejected, and has an odd number of 0 elements.

2. For the input $X = \langle 1, 0, 1, 0 \rangle$ the transitions are

$$\leadsto S_{even} \xrightarrow{X_0=1} S_{even} \xrightarrow{X_1=0} S_{odd} \xrightarrow{X_2=1} S_{odd} \xrightarrow{X_3=0} S_{even}$$

so the input is accepted, and has an even number of 0 elements.

Notes:

► Based on the fact that

1. entry actions happen when entering a given state,
2. exit actions happen when exiting a given state,
3. input actions happen based on the state and any input received, and
4. transition actions happen when a given transition between states is performed

we can categorise an FSM based on output behaviour ...

1. a **Moore** FSM only uses entry actions, i.e., the output depends on the state only, while
2. a **Mealy** FSM only uses input actions, i.e., the output depends on the state and the input

► ... or on transition behaviour, where an FSM is deemed

1. **deterministic** if for each state there is always one transition for each possible input (i.e., we always know what the next state should be), or
2. **non-deterministic** if for each state there might be zero, one or more transitions for each possible input (i.e., we only know what the next state could be).

Notes:

“Automata Theory in 10 minutes” (3)

Definition

A **Finite State Machine (FSM)** is defined by the following:

1. S , a finite set of **states** and a distinguished **start state** $s \in S$.
2. $A \subseteq S$, a finite set of **accepting states**.
3. An **input alphabet** Σ and **output alphabet** Γ .
4. A **transition function**

$$\delta : S \times \Sigma \rightarrow S.$$

5. An **output function**

$$\omega : S \rightarrow \Gamma$$

in the case of a Moore FSM, or

$$\omega : S \times \Sigma \rightarrow \Gamma$$

in the case of a Mealy FSM.


► Note that:

- The FSM itself might be enough to solve a given problem, but it is common to control an associated data-path using the outputs.
- A special “empty” input denoted ϵ allows a transition that can *always* occur.
- It’s common to allow δ to be a **partial function**, so it needn’t be defined for all inputs.
- If the FSM is non-deterministic, δ might instead give a *set* of possibilities that is randomly sampled from.

Notes:

FSMs in Hardware (1)

Algorithm

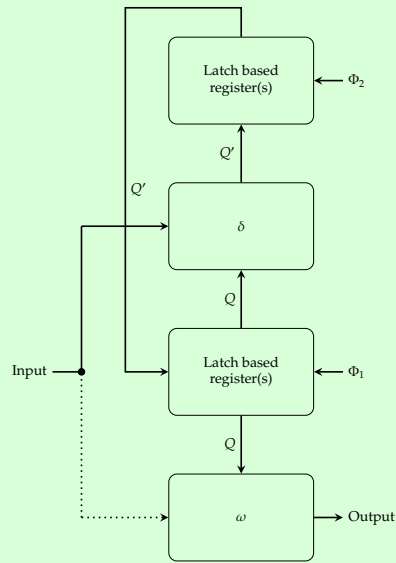

► Note that


1. δ and ω are simply combinatorial logic,
2. the state is retained in a register (i.e., a group of latches or flip-flops),
3. within the current clock cycle
 - 3.1 ω computes the output from the current state and input, and
 - 3.2 δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level or edge) in the clock

i.e., this is a framework for a *computer* we can *build*!

Notes:

FSMs in Hardware (2)

Algorithm

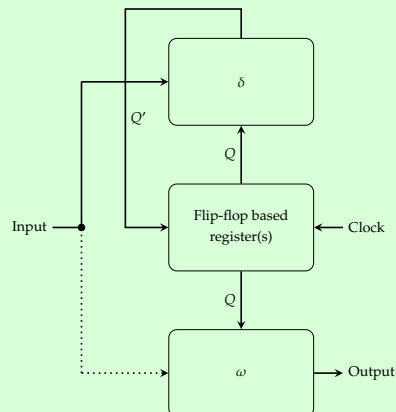

► Note that


1. δ and ω are simply combinatorial logic,
2. the state is retained in a register (i.e., a group of latches or flip-flops),
3. within the current clock cycle
 - 3.1 ω computes the output from the current state and input, and
 - 3.2 δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level or edge) in the clock

i.e., this is a framework for a *computer* we can *build*!

Notes:

FSMs in Hardware (3)

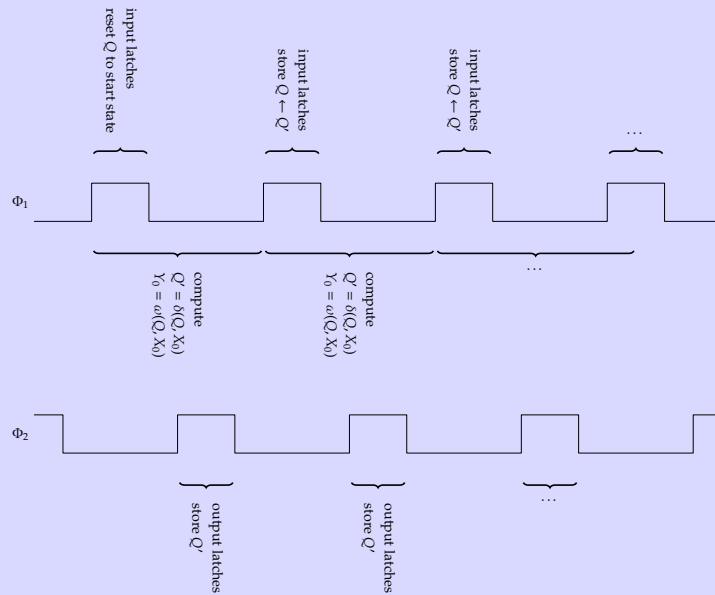
Example (given some sequence of input $X = \langle X_0, X_1, \dots \rangle$ and output $Y = \langle Y_0, Y_1, \dots \rangle$)



Notes:

FSMs in Hardware (4)

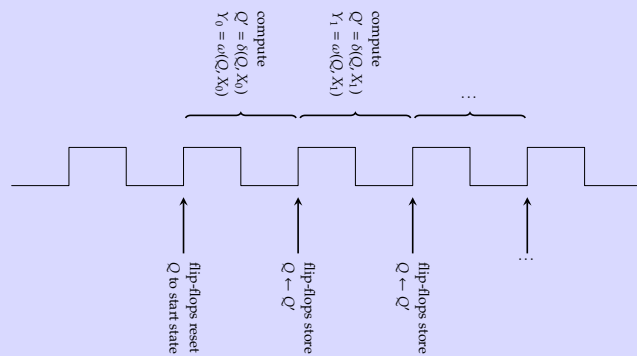Example (given some sequence of input $X = \langle X_0, X_1, \dots \rangle$ and output $Y = \langle Y_0, Y_1, \dots \rangle$)



Notes:

- ▶ To use the framework to solve a concrete problem, we follow a (fairly) standard sequence of steps:

Algorithm

1. Count the number of states required, and give each state an abstract label.
 2. Describe the state transition and output functions using a tabular or diagrammatic approach.
 3. Decide how the states will be represented, i.e., assign concrete values to the abstract labels, and allocate a large enough register to hold the state.
 4. Express the functions δ and ω as (optimised) Boolean expressions, i.e., combinatorial logic.
 5. Place the registers and combinatorial logic into the framework.
- ▶ Note that:
 - ▶ In hardware, it isn't common to have accepting states since we can't "halt"; we might include **idle** or **error** states to cope.
 - ▶ The framework doesn't show it, but in hardware it is common to have a **reset** input that (re)initialises the FSM into the start state.

Notes:

FSMs in Hardware (6) – a “modulo 6 ascending counter”

Question

Design an FSM that acts as a cyclic counter modulo n (rather than 2^n as before). If $n = 6$ for example, we want a component whose output r steps through values

$$0, 1, 2, 3, 4, 5, 0, 1, \dots,$$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).


Notes:

FSMs in Hardware (7) – a “modulo 6 ascending counter”

Algorithm (tabular)

	δ	ω
Q	Q'	r
S_0	S_1	0
S_1	S_2	1
S_2	S_3	2
S_3	S_4	3
S_4	S_5	4
S_5	S_0	5

Algorithm (diagram)

 

Notes:

FSMs in Hardware (8) – a “modulo 6 ascending counter”

- ▶ There are 6 states representing the integers $0, 1, \dots, 5$; we’ve given them the abstract labels S_0, S_1, \dots, S_5 .
- ▶ Since $2^3 = 8 > 6$, we can assign a concrete 3-bit value

S_0	\mapsto	$\langle 0, 0, 0 \rangle$
S_1	\mapsto	$\langle 1, 0, 0 \rangle$
S_2	\mapsto	$\langle 0, 1, 0 \rangle$
S_3	\mapsto	$\langle 1, 1, 0 \rangle$
S_4	\mapsto	$\langle 0, 0, 1 \rangle$
S_5	\mapsto	$\langle 1, 0, 1 \rangle$

to each abstract label; this basically means we can talk about

1. $Q = \langle Q_0, Q_1, Q_2 \rangle$ as being the current state, and
2. $Q' = \langle Q'_0, Q'_1, Q'_2 \rangle$ as being the next state.

Notes:

Algorithm (truth table)

Rewriting the abstract labels yields the following concrete truth table:


			δ			ω		
Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	r_2	r_1	r_0
0	0	0	0	0	1	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	1	0	1	0
0	1	1	1	0	0	0	1	1
1	0	0	1	0	1	1	0	0
1	0	1	0	0	0	1	0	1
1	1	0	?	?	?	?	?	?
1	1	1	?	?	?	?	?	?

Note that our state assignment means $r = Q$, so ω is basically just the identity function for that output.

Notes:

Circuit (δ)

 Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions:

$$\begin{aligned} Q'_2 &= (\quad \quad \quad Q_1 \quad \wedge \quad \quad Q_0 \quad) \vee \\ &\quad (\quad Q_2 \quad \wedge \quad \quad \quad \neg Q_0 \quad) \\ Q'_1 &= (\quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad Q_0 \quad) \vee \\ &\quad (\quad \quad \quad Q_1 \quad \wedge \quad \neg Q_0 \quad) \\ Q'_0 &= (\quad \quad \quad \neg Q_0 \quad) \end{aligned}$$

Notes:

- ▶ The fact we do state assignment late on in the process is intentional; it allows us to optimise the representation based on what we do with it.
- 1. A **binary encoding** represents the i -th of n states as a $(\lceil \log_2(n) \rceil)$ -bit unsigned integer i .
- 2. A **one-hot encoding** is where for state i , a valid code word X has $X_i = 1$ and $X_j = 0$ for $j \neq i$, e.g., for $n = 6$

S_0	\mapsto	$\langle 1, 0, 0, 0, 0, 0 \rangle$
S_1	\mapsto	$\langle 0, 1, 0, 0, 0, 0 \rangle$
S_2	\mapsto	$\langle 0, 0, 1, 0, 0, 0 \rangle$
S_3	\mapsto	$\langle 0, 0, 0, 1, 0, 0 \rangle$
S_4	\mapsto	$\langle 0, 0, 0, 0, 1, 0 \rangle$
S_5	\mapsto	$\langle 0, 0, 0, 0, 0, 1 \rangle$

noting that

- ▶ we have a larger state (i.e., n bits instead of $\lceil \log_2(n) \rceil$), **but**
- ▶ transition between states is easier, **and**
- ▶ switching behaviour (and hence power consumption) is reduced.

Notes:

FSMs in Hardware (12) – a “modulo 6 ascending/descending counter with alert”

Question

Design an FSM that acts as a cyclic counter modulo n , but whose direction can also be controlled. If $n = 6$ for example, we want a component whose output r steps through values

$0, 1, 2, 3, 4, 5, 0, 1, \dots$

or

$0, 5, 4, 3, 2, 1, 0, 5, \dots$

depending on some input d , *plus* has an output f to signal when the cycle occurs (i.e., when the current value is last or first in the sequence, depending on d).


Notes:

FSMs in Hardware (13) – a “modulo 6 ascending/descending counter with alert”

Algorithm (tabular)

Q	δ		ω		
	Q'		r	f	
	$d = 0$	$d = 1$		$d = 0$	$d = 1$
S_0	S_1	S_5	0	0	1
S_1	S_2	S_0	1	0	0
S_2	S_3	S_1	2	0	0
S_3	S_4	S_2	3	0	0
S_4	S_5	S_3	4	0	0
S_5	S_0	S_4	5	1	0

Algorithm (diagram)

 

Notes:

FSMs in Hardware (14) – a “modulo 6 ascending/descending counter with alert”

Algorithm (truth table)

Rewriting the abstract labels yields the following concrete truth table:


d	Q			δ			ω			
	Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	r_2	r_1	r_0	f
0	0	0	0	0	0	1	0	0	0	0
0	0	0	1	0	1	0	0	0	1	0
0	0	1	0	0	1	1	0	1	0	0
0	0	1	1	1	0	0	0	1	1	0
0	1	0	0	1	0	1	1	0	0	0
0	1	0	1	0	0	0	1	0	1	1
0	1	1	0	?	?	?	?	?	?	?
0	1	1	1	?	?	?	?	?	?	?
1	0	0	0	1	0	1	0	0	0	1
1	0	0	1	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0	1	0	0
1	0	1	1	0	1	0	0	1	1	0
1	1	0	0	0	1	1	1	0	0	0
1	1	0	1	1	0	0	1	0	1	0
1	1	1	0	?	?	?	?	?	?	?
1	1	1	1	?	?	?	?	?	?	?

Note that our state assignment means $r = Q$, so ω is basically just the identity function for that output.

Notes:

Circuit (δ)

 Translating the truth table into a set of Karnaugh maps




yields the following Boolean expressions:

$$\begin{aligned}
 Q'_2 &= (\neg d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad Q_0) \vee \\
 &\quad (\neg d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad \neg Q_0) \vee \\
 &\quad (\quad d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad Q_0) \vee \\
 &\quad (\quad d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad \neg Q_0) \\
 \\
 Q'_1 &= (\neg d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad Q_0) \vee \\
 &\quad (\neg d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad \neg Q_0) \vee \\
 &\quad (\quad d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad \neg Q_0) \vee \\
 &\quad (\quad d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad Q_0) \\
 \\
 Q'_0 &= (\quad \quad \quad \neg Q_0)
 \end{aligned}$$

Notes:

Circuit (ω)

 Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions:

$$\begin{aligned}
 f &= (\neg d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad Q_0) \vee \\
 &\quad (\quad d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad \neg Q_0)
 \end{aligned}$$

Notes:

► Take away points:

1. We've linked together theory and practice: FSMs are abstract computational models, but we've used them to solve concrete problems.
2. We've *only* used concepts in digital logic that we know how to construct right from the transistor-level; there is no “magic” going on behind the scenes.
3. Clearly the examples are limited, but a fundamentally similar framework can be used for more complex computational machines.

Notes:

References and Further Reading

- [1] Wikipedia: Clock signal.
http://en.wikipedia.org/wiki/Clock_signal.
- [2] Wikipedia: Finite State machine (FSM).
http://en.wikipedia.org/wiki/Finite-state_machine.
- [3] Wikipedia: Flip-flop.
[http://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics)).
- [4] Wikipedia: Latch.
[http://en.wikipedia.org/wiki/Latch_\(electronics\)](http://en.wikipedia.org/wiki/Latch_(electronics)).
- [5] D. Page.
[Chapter 2: Basics of digital logic](#).
In *A Practical Introduction to Computer Architecture*. Springer-Verlag, 1st edition, 2009.
- [6] W. Stallings.
[Chapter 11: Digital logic](#).
In *Computer Organisation and Architecture*. Prentice-Hall, 9th edition, 2013.
- [7] A.S. Tanenbaum.
[Section 3.1: Gates and Boolean algebra](#).
In *Structured Computer Organisation* [9].

Notes:

- [8] A.S. Tanenbaum.
[Section 3.2: Basic digital logic circuits.](#)
In *Structured Computer Organisation* [9].
- [9] A.S. Tanenbaum.
[Structured Computer Organisation.](#)
Prentice-Hall, 6th edition, 2012.

Notes: