

- ▶ **Problem #1:** we have latch (or flip-flop) based registers, but they aren't **addressable**.
 - ▶ An **address** (or **index**) allows dynamic rather than static reference to some stored datum.
 - ▶ By rough analogy to a C program, we have the left-hand side

Listing (C)

```
1 int A0, A1, A2, A3;  
2  
3 A0 = 0;  
4 A1 = 0;  
5 A2 = 0;  
6 A3 = 0;
```

Listing (C)

```
1 int A[ 4 ];  
2  
3 A[ 0 ] = 0;  
4 A[ 1 ] = 0;  
5 A[ 2 ] = 0;  
6 A[ 3 ] = 0;
```


but want the right-hand side.

- ▶ **Problem #2:** latches and flip-flops need a (relatively) large number of transistors per-bit; to support large capacities, it can make sense to use different components.

- ▶ There are various ways to classify a given memory component, e.g.,
 1. **Volatility**
 - ▶ **volatile**, meaning the content is lost when the component is powered-off, or
 - ▶ **non-volatile**, meaning the content is retained even after the component is powered-off.
 2. **Access type**
 - ▶ random versus constrained (e.g., sequential access to content),
 - ▶ **Random Access Memory (RAM)** which we can read from *and* write to, and
 - ▶ **Read Only Memory (ROM)** which, as suggested by the name, supports reads only.
 3. **Interface type**
 - ▶ **synchronous**, where a clock or pre-determined timing information synchronises steps, or
 - ▶ **asynchronous**, where a protocol synchronises steps.

- ▶ We're (mainly) interested in how a (volatile, synchronous) RAM component works:


Example

 

- ▶ **Goal:** a concrete implementation of *MEM* with capacity for $n = 2^{n'}$ addressable words each of w bits (where $n \gg w$).



- ▶ The EDSAC used **delay line** memory, where the rough idea is:
 - ▶ Each “line” is a tube of mercury (or something else in which sound waves propagate fairly slowly).
 - ▶ Put a speaker at one end to store sound waves into the line, and a microphone at the other to read them out.
 - ▶ Values are stored in the sense the corresponding waves take time to propagate; when they get to one end they are either replaced or fed back into the other.
- ▶ This is **sequential access** (cf. **random access**): you need to *wait* for the data you want to appear!

 

- ▶ The Whirlwind used **magnetic-core** memory, where the rough idea is:
 - ▶ The memory is a matrix of small magnetic rings, or “cores”, which can be magnetically polarised to store values.
 - ▶ Wires are threaded through the cores to control them, i.e., to store or read values.
 - ▶ The magnetic polarisation is retained, so core memory is non-volatile!
- ▶ You might still hear main memory termed **core memory** (cf. **core dump**) which is a throw-back to this technology.

Low-level Implementation (1) – SRAM and DRAM Cells

Definition (SRAM)

Static RAM (SRAM) is

- ▶ manufacturable in lower densities (i.e., smaller capacity),
- ▶ more expensive to manufacture,
- ▶ fast(er) access time (resp. lower access latency),
- ▶ easy(er) to interface with,
- ▶ ideal for use in **register files** and **cache memory**.

Definition (DRAM)


Dynamic RAM (DRAM) is

- ▶ manufacturable in higher densities (i.e., larger capacity),
- ▶ less expensive to manufacture,
- ▶ slow(er) access time (resp. higher access latency),
- ▶ hard(er) to interface with,
- ▶ ideal for use as **main memory**.

Low-level Implementation (2) – SRAM and DRAM Cells

- ▶ Abstractly, an **SRAM cell** resembles two NOT gates ...

Circuit (SRAM cell)

 


- ▶ ... concretely, we can fill in the NOT gates with the transistor-level equivalents; each “6T SRAM cell” requires 6 transistors (cf. ~ 30 or 40 for a flip-flop).

Low-level Implementation (2) – SRAM and DRAM Cells

- Abstractly, an **SRAM cell** resembles two NOT gates ...

Circuit (SRAM cell)

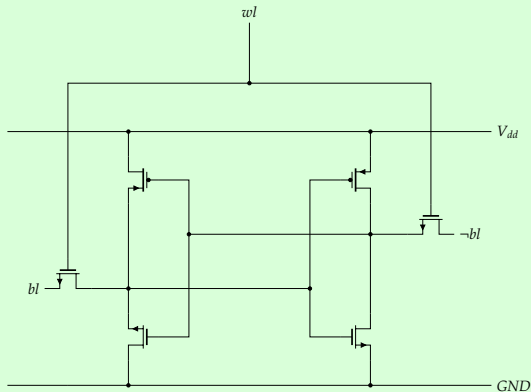


- ... concretely, we can fill in the NOT gates with the transistor-level equivalents; each “6T SRAM cell” requires 6 transistors (cf. ~ 30 or 40 for a flip-flop).

Low-level Implementation (4) – SRAM and DRAM Cells

- ▶ A **DRAM cell** is constructed using 1 transistor and a capacitor:


Circuit (DRAM cell)

 

- ▶ A **memory device** is constructed from (roughly) three components
 1. a **memory array** (or matrix) of replicated cells with
 - ▶ r rows, and
 - ▶ c columnsmeaning a $(r \cdot c)$ -cell capacity.
 2. a **row decoder** which given an address (de)activates associated cells in that row, and
 3. a **column decoder** which given an address (de)selects associated cells in that column plus additional logic to allow use (depending on cell type), e.g.,
 1. **bit line conditioning** to ensure the bit lines are strong enough to be effective,
 2. **sense amplifiers** to ensure output from the array is usable.

High(er)-level Implementation (3) – Cells \leadsto Device, SRAM

Example (an n -cell SRAM memory device)

 

High(er)-level Implementation (5) – Cells → Device, SRAM

ASI Austin Semiconductor, Inc. **SRAM MT5C1001** Limited Availability

1M x 1 SRAM SRAM MEMORY ARRAY

AVAILABLE AS MILITARY SPECIFICATIONS

- MIL-STD-883C

FEATURES

- High Speed: 20, 25, 35, and 45
- Battery Backed: 2V data retention
- Low power standby
- Single +5V (+10%) Power Supply
- Easy memory expansion with CE1 and OE1 options.
- All inputs and outputs are TTL compatible
- Three-state outputs

OPTIONS MARKING


- **Timing**
- 20ns access -20
- 25ns access -25
- 35ns access -35
- 45ns access -45
- 55ns access -55*
- 70ns access -70*

- **Package(s)**
- Ceramic DIP (400 mil) C No. 109
- Ceramic LCC BC No. 307
- Ceramic Flatpack F No. 303
- Ceramic SOJ DC3 No. 301

- **Operating Temperature Ranges**
- Industrial: -40°C to +85°C IT
- Military: -55°C to +125°C
- 2V data retention low power L

*Electrical characteristics identical to those provided for the 45ns access device.

 For more products and information
please visit our web site at
www.austinsemiconductor.com



GENERAL DESCRIPTION

The MT5C1001 employs low power, high-performance silicon-gate CMOS technology. Static design eliminates the need for external clocks or timing sources while CMOS circuitry reduces power consumption and provides for greater reliability.


For flexibility in high-speed memory applications, ASI offers chip enable (CE1) and output enable (OE1) capability. These enhancements can place the outputs in High-Z for additional flexibility in system design. Writing to these devices is accomplished when write enable (WE) remains HIGH while CE1 and OE1 go LOW. Reading is accomplished when WE remains HIGH while CE1 and OE1 go LOW. The devices offer a reduced power standby mode when disabled. This allows system designs to achieve low standby power requirements.

The "L" version provides an approximate 50 percent reduction in CMOS standby current (I_{CC1}) over the standard version.

All devices operate from a single +5V power supply and all inputs and outputs are fully TTL compatible.

ASI Austin Semiconductor, Inc. **SRAM MT5C1001** Limited Availability

FUNCTIONAL BLOCK DIAGRAM

 

TRUTH TABLE


MODE	CE1	WE	OUTPUT	POWER
STANDBY	H	X	HIGH-Z	STANDBY
READ	L	H	O	ACTIVE
WRITE	L	L	WRTN-Z	ACTIVE

PIN ASSIGNMENTS

PIN	ASSIGNMENT
A ₀ -A ₁₅	Address Inputs
WE1	Write Enable
CE1	Chip Enable
D	Data Input
Q	Data Output
NC	No Connection
V _{CC}	+5V Power Supply
V _{DD}	Ground

High(er)-level Implementation (7) – Cells \leadsto Device, DRAM

Example (a n -cell DRAM memory device)

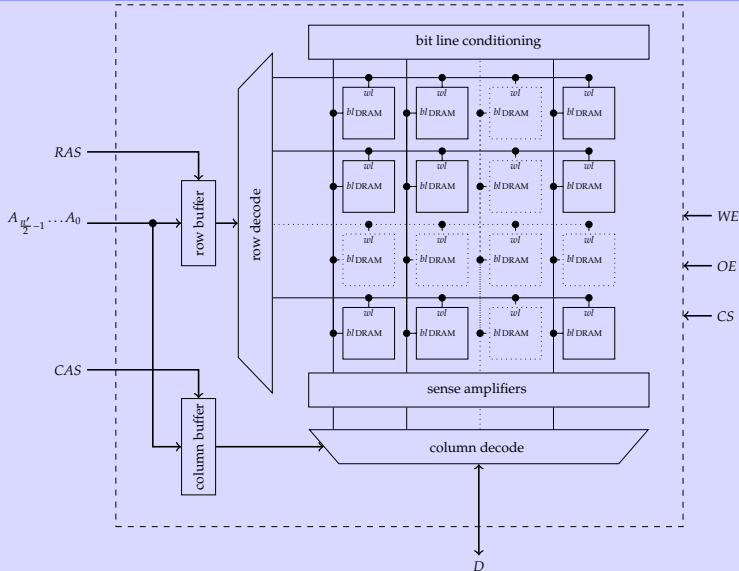

High(er)-level Implementation (9) – Cells → Device, DRAM

ASi AUSTIN SEMICONDUCTOR, INC.

MT4C1004J 883C
4 MEG x 1 DRAM

DRAM

4 MEG x 1 DRAM

FAST PAGE MODE

AVAILABLE AS MILITARY

SPECIFICATIONS

- STD. 883C 8832
- MIL-STD-883

FEATURES

- Industry standard x1 pinout, timing, functions and packages
- High performance, CMOS efficient gate process
- Single +5V ±10% power supply
- Low power, 1.5mW standby, 300mW active, typical
- All inputs, outputs and clocks are fully TTL and CMOS compatible
- 1.8M-cycle refresh distributed across 16ms
- Refresh modes: **EAS-ONLY**, **CAS-BEFORE-EAS** (CBE), and **HIDDEN**
- **FAST PAGE MODE** access cycle
- **CBE** with **WE** a **HIGH** (BEC) test mode capable via **WCBE**


OPTIONS

MARKING

Timing	- 7
90ns access	- 8
100ns access	- 10
110ns access	- 12
Packages	
Ceramic DIP (D88 mil)	CN No. 101
Ceramic DIP (100 mil)	C No. 102
Ceramic LCC	ECN No. 103
Ceramic SOJ	ECJ No. 104
Ceramic ZIP	CZ No. 105
Ceramic Gull Wing	ECG No. 106

GENERAL DESCRIPTION

The MT4C1004J is a randomly accessed solid-state memory containing 4,194,304 bits organized in a x1 configuration. During **READ** or **WRITE** cycles, each bit is uniquely addressed through the 22 address lines which are entered 11 bits (A0-A10) as true **EAS** and in the next 11 bits (A11-A21) as **CAS** the latter 11 bits, a **READ** or **WRITE** cycle is selected with the **WE** input. A logic **HIGH** on **WE** denotes **READ** mode while a logic **LOW** on **WE** denotes **WRITE** mode. During a **WRITE** cycle, data in **D** is latched by the

 

*Numbers not used for **EAS-ONLY** REFRESH

falling edge of **WE** or **CAS**, whichever occurs last. If **WE** goes **LOW** prior to **CAS** going **LOW**, the output pins remain open (**High Z**) until the next **CAS** cycle. If **WE** goes **LOW** after data reaches the output **Q**, **Q** is activated and retains the selected cell data as long as **CAS** remains **LOW** (regardless of **WE** or **EAS**). This **LATE** **WE** pulse results in a **READ**, **WRITE** cycle. **FAST PAGE MODE** operations allow faster data operations **READ**, **WRITE** or **READ-MODIFY-WRITE** within a row address (**A0-A10**) defined page

2-23


ASi AUSTIN SEMICONDUCTOR, INC.

MT4C1004J 883C
4 MEG x 1 DRAM

boundary. The **FAST PAGE MODE** cycle is always initiated with a row address strobed in by **EAS** followed by a column address strobed in by **CAS**. **CAS** may be toggled in by holding **EAS** **LOW** and strobing to different column addresses, thus executing faster memory cycles. Terminating **EAS** **HIGH** terminates the **FAST PAGE MODE** operation. Reasserting **EAS** and **CAS** **HIGH** terminates a memory cycle and decreases chip current to a reduced standby level. Also,

the chip is pre-conditioned for the next cycle during the **EAS** **HIGH** time. Memory cell data is retained in its correct state by maintaining power and no waiting on **EAS** cycle **BREAD**, **WRITE**, **EAS-ONLY**, **CAS-BEFORE-EAS** or **HIDDEN** REFRESH so that all 1.8M combinations of **EAS** addresses (**A0-A10**) are executed at least every time, regardless of sequence. The **CAS-BEFORE-EAS** cycle will invoke the refresh counter for automatic **EAS** addressing.

FUNCTIONAL BLOCK DIAGRAM FAST PAGE MODE

 


NOTE: **WE** **LOW** prior to **CAS** **LOW**, **EW** detection circuit output is a **HIGH** (EARLY-**WRITE**)
CAS **LOW** prior to **WE** **LOW**, **EW** detection circuit output is a **LOW** (LATE-**WRITE**)

2-24


High(er)-level Implementation (11) – Cells \leadsto Device

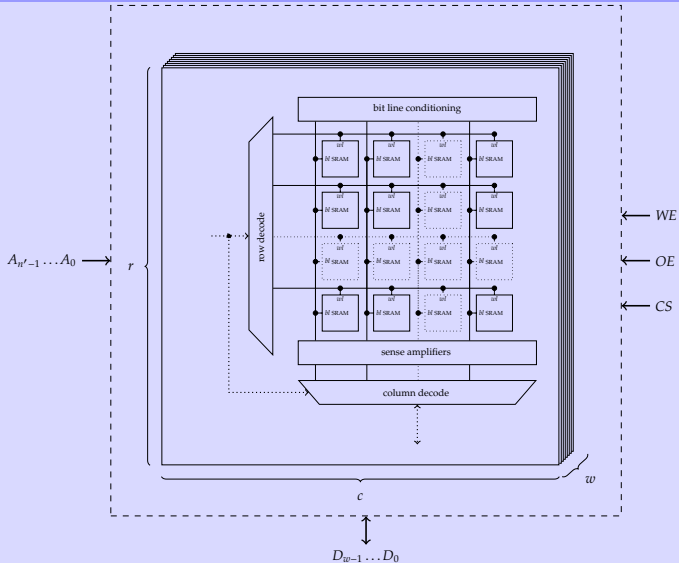Example (from a 1-bit to w -bit SRAM device via replication)



An Aside: “what about ROM devices?”

Example (an n -cell ROM memory device)

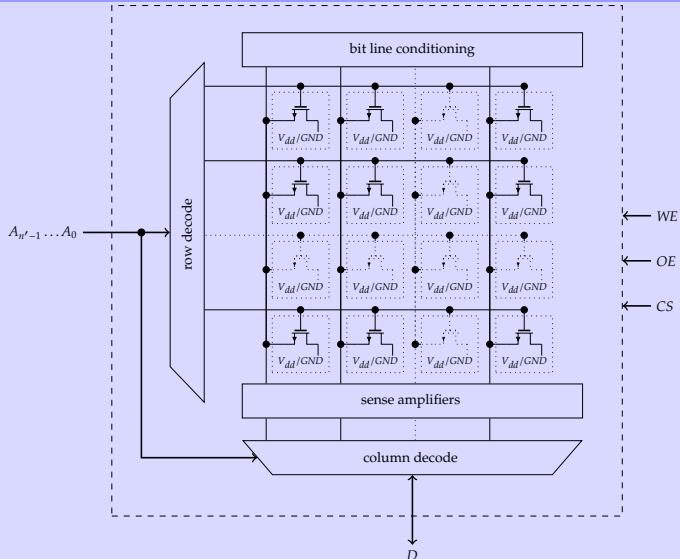

► Take away points:

1. The initial goal was an n -element memory of w -bit words; the final solution is motivated by divide-and-conquer, i.e.,
 - 1.1 one or more channels, each backed by
 - 1.2 one or more physical banks, each composed from
 - 1.3 one or more devices, each composed from
 - 1.4 one or more logical banks, of
 - 1.5 one or more arrays, of
 - 1.6 many cells
2. The major complication is a large range of increasingly detailed options:
 - lots of parameters mean lots of potential trade-offs (e.g., between size, speed and power consumption),
 - need to take care of detail: there are so many cells, any minor change can have major consequences!
3. Even so, there is just one key concept: we have some cells, and however they are organised we just need to identify and use the right cells given some address.

References and Further Reading

- [1] Wikipedia: Computer memory.
http://en.wikipedia.org/wiki/Category:Computer_memory.
- [2] Wikipedia: Dynamic random access memory.
http://en.wikipedia.org/wiki/Dynamic_random-access_memory.
- [3] Wikipedia: Memory geometry.
http://en.wikipedia.org/wiki/Memory_geometry.
- [4] Wikipedia: Static random access memory.
http://en.wikipedia.org/wiki/Static_random_access_memory.
- [5] U. Drepper.
[What every programmer should know about memory.](http://www.akkadia.org/drepper/cpumemory.pdf)
<http://www.akkadia.org/drepper/cpumemory.pdf>.
- [6] D. Page.
[Chapter 8: Memory and storage.](#)
In *A Practical Introduction to Computer Architecture*. Springer-Verlag, 1st edition, 2009.
- [7] W. Stallings.
[Chapter 5: Internal memory.](#)
In *Computer Organisation and Architecture*. Prentice-Hall, 9th edition, 2013.
- [8] A.S. Tanenbaum.
[Section 3.3.4: Memory organisation.](#)
In *Structured Computer Organisation* [11].

References and Further Reading

- [9] A.S. Tanenbaum.
[Section 3.3.5: Memory chips.](#)
In *Structured Computer Organisation* [11].
- [10] A.S. Tanenbaum.
[Section 3.3.6: RAMs and ROMs.](#)
In *Structured Computer Organisation* [11].
- [11] A.S. Tanenbaum.
[Structured Computer Organisation.](#)
Prentice-Hall, 6th edition, 2012.