

- **Recall:** our goal is to implement a bit-serial multiplier, i.e.,

Algorithm

Input: Two unsigned, n -bit, base-2 integers x and y


Output: An unsigned, $2n$ -bit, base-2 integer
 $r = y \cdot x$

```

1  $t \leftarrow 0$ 
2 for  $i = n - 1$  downto 0 step -1 do
3    $t \leftarrow 2 \cdot t$ 
4   if  $y_i = 1$  then
5      $t \leftarrow t + x$ 
6   end
7 end
8 return  $t$ 

```

Circuit

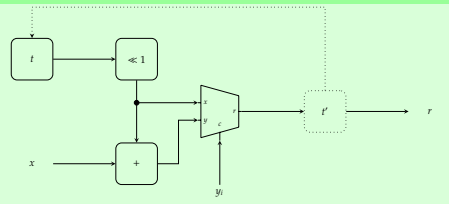

as a case-study of data- and control-paths; we more or less have the data-path, but what about the control-path ...

Question

Design an FSM-based component that replicates the behaviour of a loop counter, for example `i` within a C-style `for` loop such as

```
1 for( int i = m; i < n; i++ ) {  
2   ...  
3 }
```

noting that


1. like C, we'll allow the loop counter `i` to equal `n` once the loop is complete,
2. we'll need a mechanism that informs us when this is, plus also allows us to start iteration, and
3. we'll look at *a* solution, not *all* solutions.

An Aside: A simple, generic control protocol

- ▶ **Question:** given a user C_1 of some component C_2 , how does
 1. C_2 know when to start computation (e.g., when any input x is available), and
 2. C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- ▶ **Solution(s):**
 1. use a shared clock signal to synchronise events somehow, **or**
 2. use a simple **control protocol** based on two signals
 - 2.1 *req* (or **request**), and
 - 2.2 *ack* (or **acknowledge**).


An Aside: A simple, generic control protocol

Algorithm

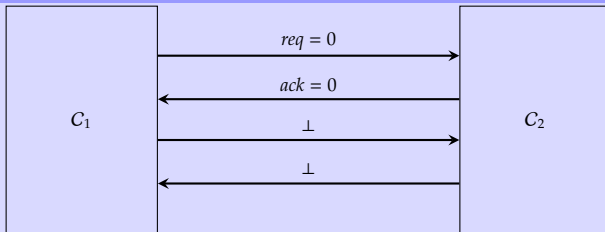


An Aside: A simple, generic control protocol

Algorithm

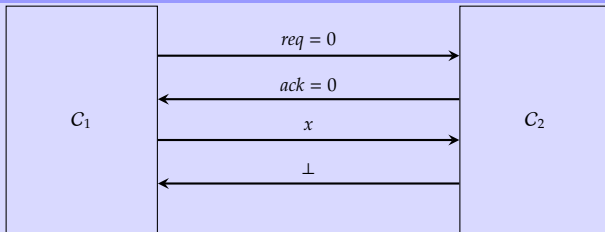


An Aside: A simple, generic control protocol

Algorithm

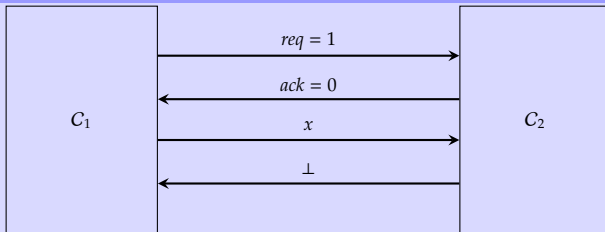


An Aside: A simple, generic control protocol

Algorithm

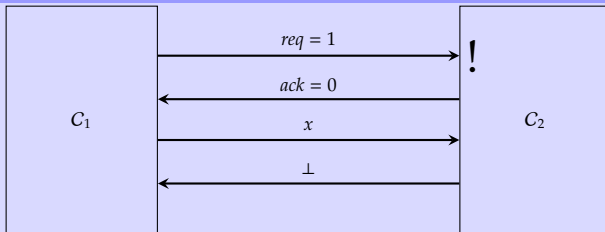


An Aside: A simple, generic control protocol

Algorithm

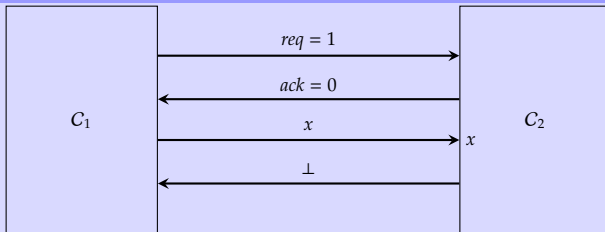


An Aside: A simple, generic control protocol

Algorithm

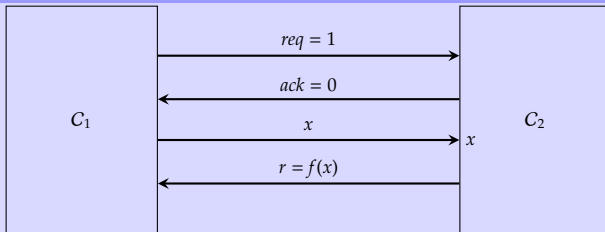


An Aside: A simple, generic control protocol

Algorithm

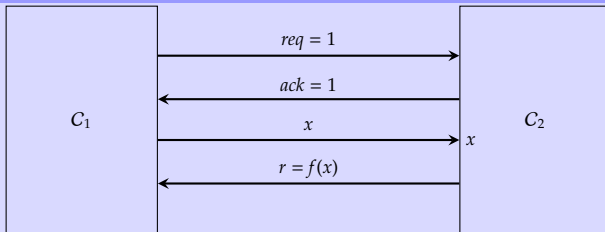


An Aside: A simple, generic control protocol

Algorithm

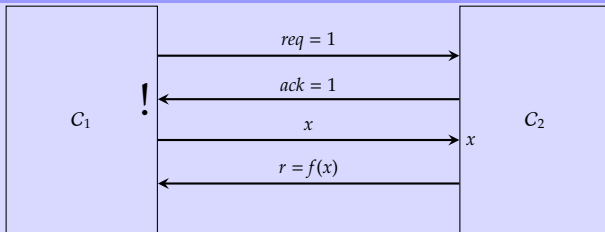


An Aside: A simple, generic control protocol

Algorithm

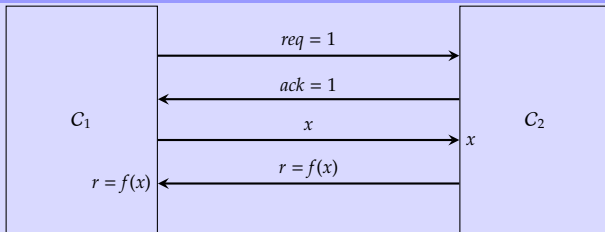


An Aside: A simple, generic control protocol

Algorithm

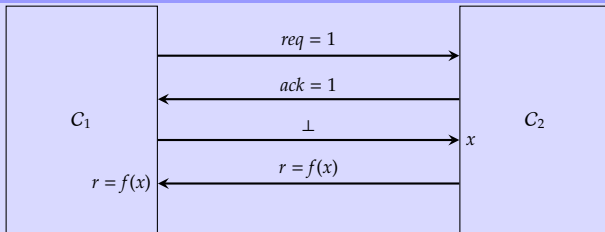


An Aside: A simple, generic control protocol

Algorithm

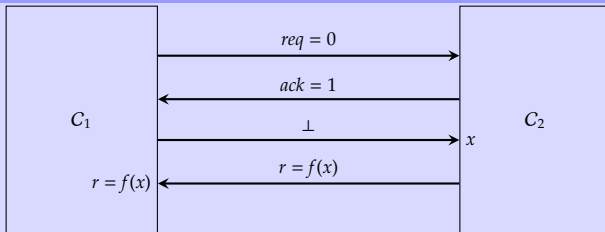


An Aside: A simple, generic control protocol

Algorithm

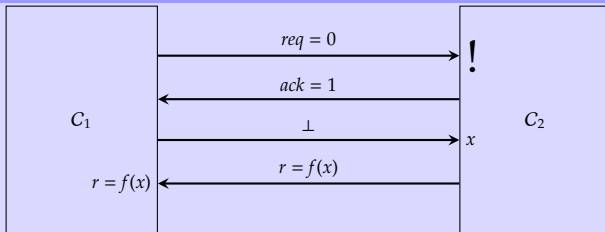


An Aside: A simple, generic control protocol

Algorithm

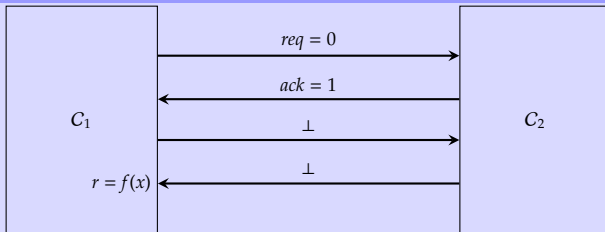


An Aside: A simple, generic control protocol

Algorithm

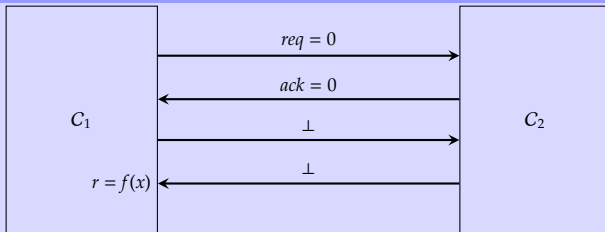


An Aside: A simple, generic control protocol

Algorithm

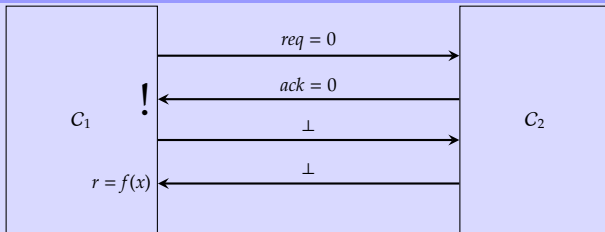


An Aside: A simple, generic control protocol

Algorithm

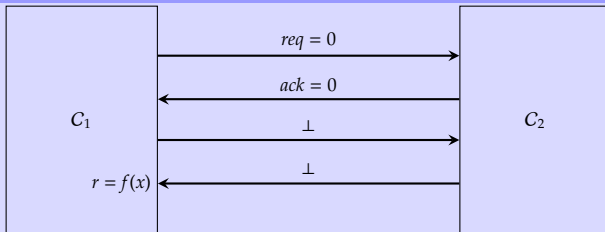

A controlled “loop counter” component (1)

Circuit (data-path, sketch)

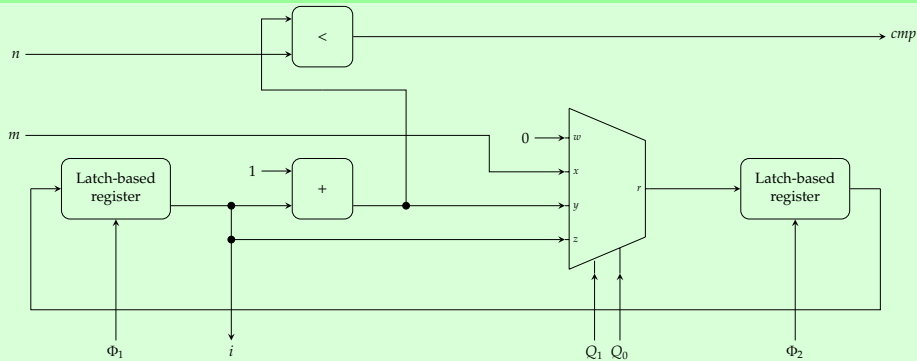

A controlled “loop counter” component (2)

- ▶ Our FSM can be in one of 4 states:
 - ▶ in S_{wait} it waits for a request (i.e., for $req = 1$),
 - ▶ in S_{init} it uses any input to initialise itself (e.g., setting the initial loop counter value),
 - ▶ in S_{step} it performs an iteration of the loop, and
 - ▶ in S_{done} it waits for $req = 0$ (while setting $ack = 1$) once the loop is complete.
- ▶ Since $2^2 = 4$, we can assign a concrete 2-bit value

S_{wait}	\mapsto	$\langle 0, 0 \rangle$
S_{init}	\mapsto	$\langle 1, 0 \rangle$
S_{step}	\mapsto	$\langle 0, 1 \rangle$
S_{done}	\mapsto	$\langle 1, 1 \rangle$

to each abstract label; this basically means we can talk about

1. $Q = \langle Q_0, Q_1 \rangle$ as being the current state, and
2. $Q' = \langle Q'_0, Q'_1 \rangle$ as being the next state.

A controlled “loop counter” component (3)

Algorithm (control-path, tabular)


Algorithm (control-path, diagram)

A controlled “loop counter” component (3)

Algorithm (control-path, tabular)

		δ		ω	
Q		Q'		ack	
		$cmp = 0$	$cmp = 1$	$cmp = 0$	$cmp = 1$
$req = 0$	S_{wait}	S_{wait}	S_{wait}	0	0
	S_{init}	S_{wait}	S_{wait}	0	0
	S_{step}	S_{wait}	S_{wait}	0	0
	S_{done}	S_{wait}	S_{wait}	1	1
$req = 1$	S_{wait}	S_{init}	S_{init}	0	0
	S_{init}	S_{step}	S_{step}	0	0
	S_{step}	S_{done}	S_{step}	0	0
	S_{done}	S_{done}	S_{done}	1	1

Algorithm (control-path, diagram)

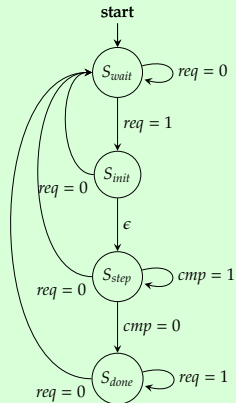

A controlled “loop counter” component (4)

Algorithm (control-path, truth table)

Rewriting the abstract labels yields the following concrete truth table:

<i>req</i>	<i>cmp</i>			δ		ω
		Q_1	Q_0	Q'_1	Q'_0	<i>ack</i>
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	0	1	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	1

A controlled “loop counter” component (5)

Circuit (control-path, δ)


Translating the truth table into a set of Karnaugh maps

yields the following Boolean expressions:

A controlled “loop counter” component (5)

Circuit (control-path, δ)

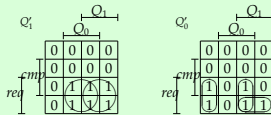Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions:

$$Q_1' = (req \wedge \neg cmp \wedge \neg Q_0) \vee (req \wedge cmp \wedge \neg Q_1)$$

$$Q_0' = (req \wedge \neg cmp \wedge \neg Q_1) \vee (req \wedge cmp \wedge \neg Q_0) \vee (req \wedge \neg cmp \wedge Q_1)$$

A controlled “loop counter” component (6)

Circuit (control-path, ω)

Translating the truth table into a set of Karnaugh maps

yields the following Boolean expressions:

A controlled “loop counter” component (6)

Circuit (control-path, ω)

Translating the truth table into a set of Karnaugh maps


	Q_1	Q_0
ack	0	1
	0	0
	0	1
	1	0
	1	1
req	0	1
	0	0
	1	0
	1	1

yields the following Boolean expressions:

$$ack = Q_1 \wedge Q_0$$


A controlled “loop counter” component (7)

Circuit (data-path, finalised)

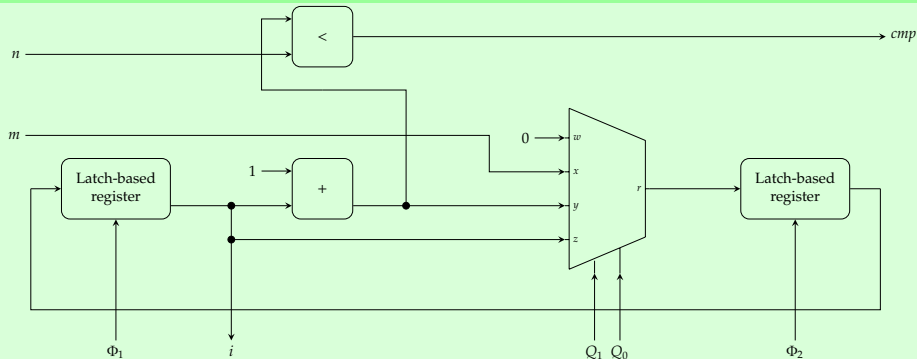

A controlled “loop counter” component (8)

Circuit (data- and control-paths)

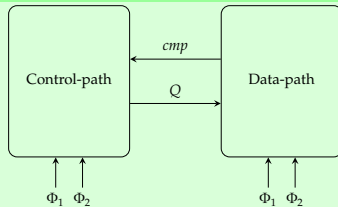

Demo and discussion

- ▶ **Next steps** (or, the lab. session):
 - ▶ We now have the loop counter component implemented as specified ...
 - ▶ ... the next challenge is clearly then *using* it to realise the original goal, e.g., specifying
 1. any additional data-path components required, and
 2. how loop counter (the control-path) controls themso we end up with a bit-serial multiplier.